

# DIGITAL VLSI

## LAB ASSIGNMENT 1

Problem 1: NMOS and PMOS plots using Cadence.

In this exercise, you are required to generate both NMOS and PMOS I-V device characteristics (I/P and O/P) using Cadence (Use 65nm process Technology). Plot your results. Compare the current levels for the two devices in saturation when they are minimum sized.


Now connect the PMOS and NMOS transistors to form a CMOS inverter. Plot the voltage transfer characteristics, and observe the variation by varying the pull-up to pull-down device ratios. Please report the width of the PMOS for which symmetric switching is achieved. Calculate the Noise Margin in the form of NML and NMH from plot.

Solution:

**NMOS:** N type MOSFET is formed by taking p substrate and two high doped n is diffused in this p substrate. These two are taken as drain and source. Between drain and source channel is formed. NMOS is in the cut off region when gate to source voltage ( $V_{gs}$ ) is negative. So for enhancement mode  $V_{gs}$  is greater than threshold voltage.


Doing in cadence we give positive supply to gate and drain. Value of this positive supply is 1.2V (Because we are working in 65nm process technology so that the maximum supply voltage is 1.2V). we do the analysis in the range of 0 to 1.2V.

### Schematic diagram of NMOS in Cadence

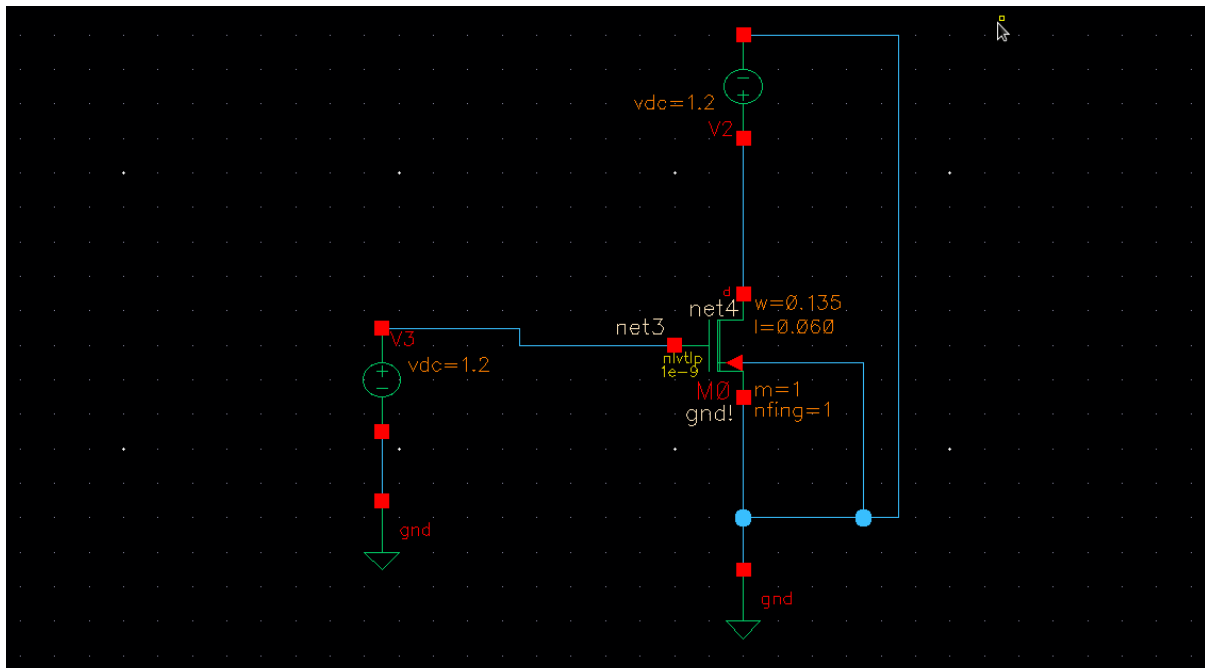


Two different types of analysis:

 - 1) Curve B/W  $I_d$  and  $V_{ds}$  Taking  $V_{gs}$  constant (1.2V). (Output characteristics). It comes in 1<sup>st</sup> quadrant.



 
- 2). Curve B/W  $I_d$  and  $V_{gs}$  Taking  $V_{ds}$  constant(1.2V) (Input characteristics). This comes in 1<sup>st</sup> quadrant.



## PMOS:

PMOS is behaving just opposite to NMOS. PMOS is made by taking N type substrate and doped TWO high doped P in N type substrate. PMOS is working when gate to source voltage is negative. So in this analysis we apply negative voltage to gate and drain. Also do it analysis to -1.2 to 0.


### Schematic of PMOS in cadence

 

We do analysis of two types:

 
1). Curve B/W  $I_d$  and  $V_{ds}$  Taking  $V_{gs}$  constant. (Output characteristics)

This curve is B/W  $I_d$  and  $V_{ds}$  for different values of  $V_{gs}$  (-1.2 to 0 linear steps 4). Values of  $V_{gs}$  is varies by taking a variable and do it simulation. Characteristic is come 3<sup>rd</sup> quadrant.



 2). Curve B/W  $I_d$  and  $V_{gs}$  Taking  $V_{ds}$  constant.( input characteristics)


This curve is B/W  $I_d$  and  $V_{gs}$  for different values of  $V_{ds}$  (-1.2 to 0 linear steps 4). The characteristic is come 3<sup>rd</sup> quadrant.




## CMOS INVERTER:

CMOS INVERTER is combination of NMOS and PMOS. NMOS is used as a pull down system and PMOS is used as a pull up system. The output is inverse of the input which is given to CMOS inverter. In CMOS we give  $V_{gs}$  and  $V_{ds}$  as 1.2V. In B/W the NMOS and PMOS we take the output.

## Schematic of CMOS Inverter:

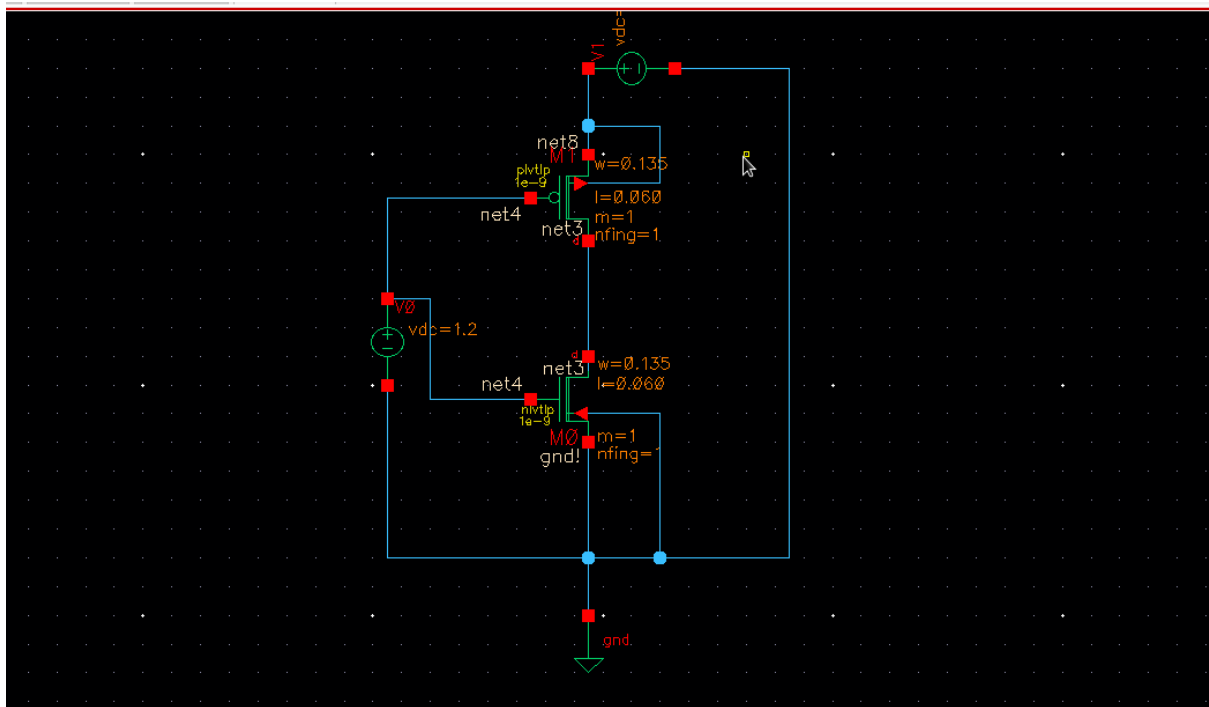


 We analysis the transfer characteristics.(  $V_{out}$  v/s  $V_{in}$  ).




Then take a variable which varies the width of PMOS and do the analysis where symmetric switching is obtained (at symmetric switching  $V_{in}=V_{out}=V_{dd}/2$  is occur so we at that width ratio which is nearest to this point).

Transfer characteristics:

 

I take a variable PMOS width= $w$  and sweep it firstly 0 to 4 and then i plot a graph than for exact calculation i take  $w = 2.5$  to  $2.75$  and sweep it taking linear step of 6. Then I found for approximate symmetric switching I get 2.625 width ratio of PMOS to NMOS.

 Approximate switching width ratio 2.625. For Noise margin we take the points where slope -1 and 1. We take that point and calculate the noise margin:



Where slope is -1.

$V_{oh}=V_{out} = 1.06 \text{ V}$

$V_{il}=V_{in}= 0.514$

Where slope is 1

$V_{ol}=V_{out}= .129$

$V_{in}=0.68\text{V}$

Noise margin  $N_{low}$

Noise Margin  $N_{high}$

2. (a) Analyze and plot  $V_{out}$  vs.  $V_{in}$  with  $V_{in}$  varying from 0 to 1.2 volts (use steps of 0.25 V) for the MOS circuit shown below. Consider  $V_{DD}= 1.2 \text{ V}$ .

(b) Repeat (a) using Cadence.


c) Repeat (a) and (b) using a MOS transistor with  $(W/L) = 3/1$ . While doing so, vary the resistance values and report the results for 16K, 32K, and 64K Ohms. Is the discrepancy between manual and computer analysis larger or smaller (perform hand calculations for only resistance 64K)? Explain why. Also plot the voltage transfer characteristics and comment on noise margins. Can this circuit be used as an inverter?

Solution:

**Using Cadence:** firstly I do with 8K resistor and draw the transfer characteristics

Schematic characteristic:


vgs

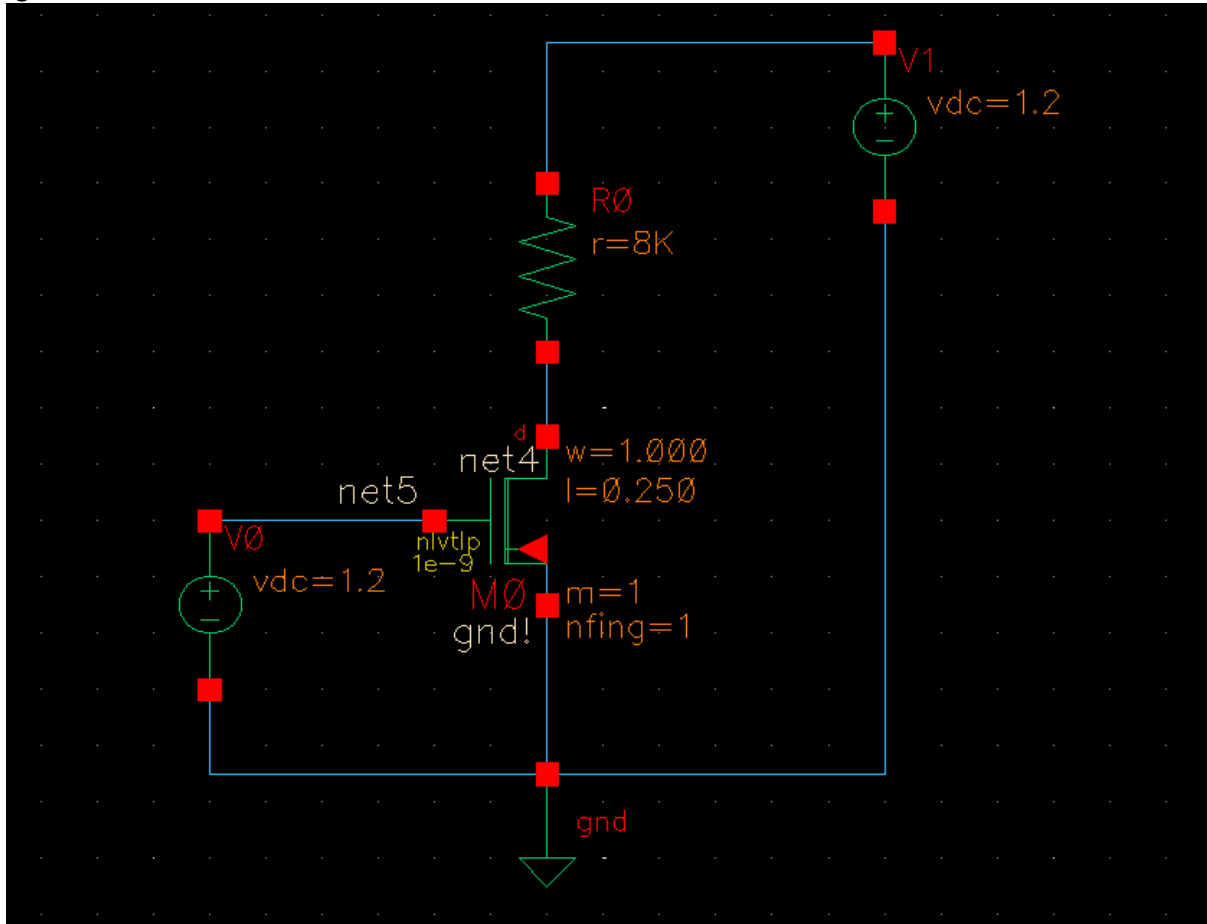

i take Vgs and vds is equal to 1.2V and do simple analysis by which i can get transfer charcterstics of this circuit.



 
Transfer Characteristics for taking  $V_{out}$  v/s  $V_{in}$  taking Step Size of  $V_{in}$  is 0.25:



For question (c) change the width ratio by 3/1 mean width of NMOS is multiplied by 3. And take the resistor as a variable and varies it from 8 to 64 by taking times stepping of 2. So we get these types of transfer characteristics graph for 8K, 16K, 32K, 64K ohm resistor. also take  $V_{ds}$  is taking in step size of 0.25.


As the resistance increases switching characteristics is decreases mean 64K is most away from its switching characteristics. As the resistance increases graph goes down.

 No this circuit can't be used as inverter because for 8K ohm resistor  $V_{out}$  does not goes to Zero. As the resistance increases  $V_{out}$  goes towards to zero. But not exact to be zero. So this circuit cannot behave like inverter.



(a).manual calculation of a and c part:

(9)

 

Vijay Sharma  
MT14035

Three Region For MOSFET.

① Triode Region / linear Region (edge of)  $t_{ox} = 1.2 \text{ nm}$

$$V_{ds} = V_{as} - V_{th}$$

$$V_{out} - 0 = V_{in} - 0 - V_{th}$$

$$V_{out} = V_{DD} - I_D R_D$$

$$V_{out} = V_{in} - V_{th}$$

$$V_{out} = V_{DD} - I_D R_D$$

$$= 1.2 - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{th})^2 \times R_D$$

$$= 1.2 - \frac{7.47 \times 10^{-3}}{4} (V_{in} - V_{th})^2 \times R_D$$

$$V_{out} = 1.2 - \frac{7.4 \times 8}{4} (V_{in} - V_{th})^2$$

$$V_{out} = V_{in} - V_{th}$$

$$V_{in} - 0.3 = 1.2 - \frac{7.4 \times 8}{4} (V_{in} - V_{th})^2$$

$$V_{in} = 1.5 - \frac{7.4 \times 8}{4} (V_{in} - V_{th})^2$$

~~$$V_{in} = 1.5 - 15 (V_{in} - V_{th})^2$$~~

$$V_{in} = 1.5 - 15 (V_{in} - V_{th})^2$$

$$V_{in} = 1.5 - 15 (V_{in} - 0.3)^2$$

For 65 nm Process

$$V_{th} = 0.3 \text{ V}$$

For Saturation Region

$$I_D = \frac{1}{2} \mu_n C_{ox} (V_{as} - V_{th})^2$$

$$W/L = 1/0.25 = 4$$

$$\mu_n C_{ox} \frac{W}{L}$$

$$= \frac{650 \times 10^{-4}}{2} \times \frac{\epsilon_{ox}}{t_{ox}} \times \frac{W}{L}$$

$$= \frac{650 \times 10^{-4}}{2} \times \frac{3.9 \times 8.85 \times 10^{-12}}{1.2 \times 10^{-9}}$$

$$= 3.73 \times 10^{-3}$$

$$V_{in} = 1.5 - 15 (V_{in} - 0.3)^2$$

$$V_{in} = 1.5 - 15 (V_{in}^2 + 0.09 - 0.6 V_{in})$$

Solving this quad. eqn of  $V_{in}$  i get

$$\cancel{V_{in} = 0.55 V}. V_{in} = 0.55 V. (\text{approx})$$

$$V_{out} = V_{in} - V_{th}$$

$$= 0.55 - 0.3 = 0.25 V.$$

Triode Region

$$V_{in} > 0.55 V$$


Saturation Region

$$0.3 < V_{in} < 0.55$$

Cutoff Region

$$V_{in} < 0.3 V$$

$$V_{out} = 1.2 V.$$

 

Transfer Characteristics at 8K Resistor.

Max value of  $V_{out} = 1.2V$



③ In the same last question if we take  
edge of Triode  $\frac{W}{L} = 3$  and  $R_D = 64 \text{ k}\Omega$ .

$$V_{out} = V_{in} - V_{th} \quad (V_{DS} = V_{DS} - V_{th})$$

$$V_{in} - 0.3 = 1.2 - \frac{1}{2} \times \frac{650 \times 10^{-4} \times 3.9 \times 10^{-12} \times 885}{1.2 \times 10^{-9}} \times 3 \times \frac{64}{10^3}$$

Solving this quadratic eqn.  $(V_{in} - 0.3)^2$

$$V_{in} = 0.45 \text{ V.}$$

So at this Voltage  $V_{out} = V_{in} - V_{th}$   
 $= 0.45 - 0.3$   
 $= 0.15$

Triode Region	Saturation Region	Cutoff Region
$V_{in} > 0.45$	$0.3 < V_{in} < 0.45$	$V_{in} < 0.3 \text{ V.}$
$V_{out} = 0.15$		

